






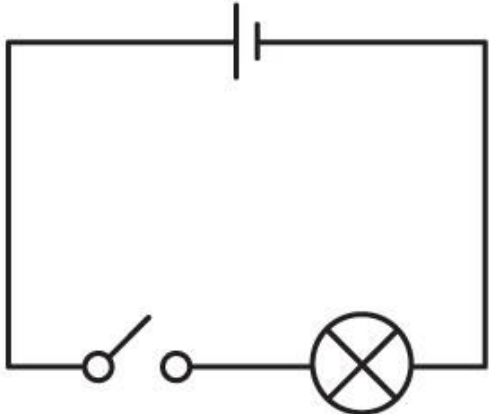




## Springbank Primary School Knowledge Organiser



<b>Year 4</b>	<b>Term: Autumn term 2</b>	<b>Focus - Electricity</b>
---------------	----------------------------	----------------------------

Vocabulary	Definitions	Diagrams
<b>Circuit</b>	An electrical circuit is a complete pathway that an electrical current can flow around. Electrical current is the flow of electrons which are negatively charged particles. A circuit needs a power source and an unbroken path for the current to flow.	<p><b>Electrical circuit symbols</b></p> <div style="display: flex; justify-content: space-around; align-items: flex-start;"> <div style="text-align: center;">   <b>Battery</b> </div> <div style="text-align: center;">   <b>Wire</b> </div> <div style="text-align: center;">   <b>Bulb</b> </div> <div style="text-align: center;">   <b>Buzzer</b> </div> </div> <div style="display: flex; justify-content: space-around; align-items: flex-start; margin-top: 10px;"> <div style="text-align: center;">   <b>Motor</b> </div> <div style="text-align: center;">   <b>Switch (off)</b> </div> <div style="text-align: center;">   <b>Switch (on)</b> </div> </div> <p><b>A circuit diagram</b></p>  <p style="text-align: center;"><b>Battery</b></p> <p style="text-align: right; margin-right: 20px;"><b>Wire</b></p> <p style="text-align: center;"><b>Switch (off)</b>      <b>Bulb</b></p>
<b>Cell/battery</b>	A cell is a power source; it is a store of energy. Multiple cells connected together make a battery. It gives the electrons that are everywhere in the circuit a push so that they can move around the circuit. Cells/batteries run out of power when all their stored energy has been used up.	
<b>Wire</b>	Wires are lengths of plastic covered metal with metal connectors at the ends. They are used to join components in a circuit.	
<b>Bulb</b>	A bulb is an electrical component that lights up when an electrical current passes through it.	
<b>Buzzer</b>	A buzzer is an electrical component that makes a sound up when an electrical current passes through it.	
<b>Motor</b>	A motor is an electrical component that spins when an electrical current passes through it.	
<b>Switch</b>	A switch is part of an electrical circuit that can be opened or closed to control the flow of electricity. If a switch is open (off) there is a break in the circuit and the current cannot flow. If the switch is closed (on) then the circuit is complete and the current can flow around the circuit.	
<b>Conductors</b>	Electrical conductors are materials that allow an electrical current to flow through them. All metals such as copper, iron and steel plus graphite are conductors.	
<b>Insulators</b>	Insulators are materials that do not allow electrical current to flow through them. Wood, plastic and rubber are all insulators.	
<b>Appliances</b>	Appliances are machines that use electricity, some use mains electricity and others run on batteries.	